

Design of a simple 8-bit Microprocessor

One of my key RTL projects was the **design of a simple 8-bit microprocessor** as part of my VLSI laboratory coursework. The microprocessor supported six registers (A–F) and implemented a small instruction set with five operations: **ADD, SUB, MOV, IN, and OUT**. The design used an 8-bit input bus, an 8-bit output bus, and 8-bit instruction codes.

The project involved building the datapath and control modules in Verilog, including:

- A **3-to-8 decoder** for register selection.
- An **adder/subtractor unit** for arithmetic operations.
- An **ALU module** to handle instruction decoding and execution.
- A **microprocessor top module** integrating registers, control logic, and data path.
- A **testbench** to verify correct functionality with various instruction sequences.

My role in the project included:

- Writing the Verilog RTL for the ALU, decoder, and microprocessor integration.
- Debugging issues related to data hazards and synchronization. Initially, the design latched onto incorrect values due to improper clocking, which I resolved by introducing a positive edge-triggered clocking scheme.
- Implementing pipelining in the microprocessor, ensuring data and control signals were properly staged across cycles.
- Creating the testbench, running simulations, and analyzing waveforms to validate the design using Vivado.

Through this project, I gained hands-on experience with RTL design, debugging hazards, and writing verification environments, as well as practical understanding of how a simple processor datapath is implemented in hardware.

Objective:


Design a sample microprocessor with 6 registers and 5 operations. Input bus and Output bus need to be of 8-bit width. The instruction set consists of 8-bit instructions. The allowed operations are ADD, SUB, MOV, IN and OUT.

Assume the 6 registers as A, B, C, D, E and F. Say R, R1 and R2 is used to represent one of the registers. The operations are defined as follows.



- **ADD R:** Add the value in R to value in A and update A to the obtained sum.
- **MOV R1 R2:** Copy the value of R2 into R1.
- **IN R:** Input an 8-bit number to register R.
- **OUT R:** Output the 8-bit number in register R.

Assign 8-bit instructions to each of the above 5 operations.

Architecture

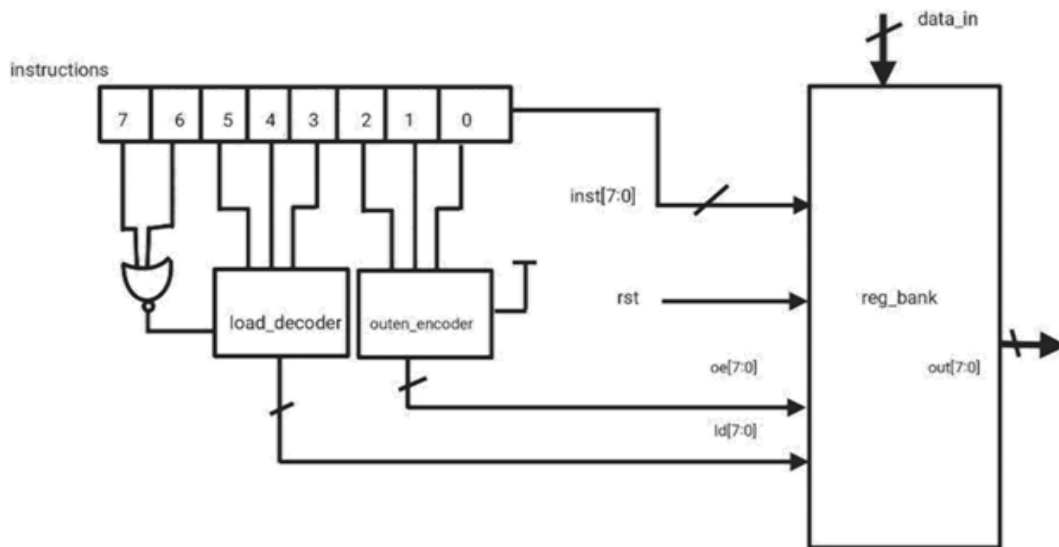

Main Architecture

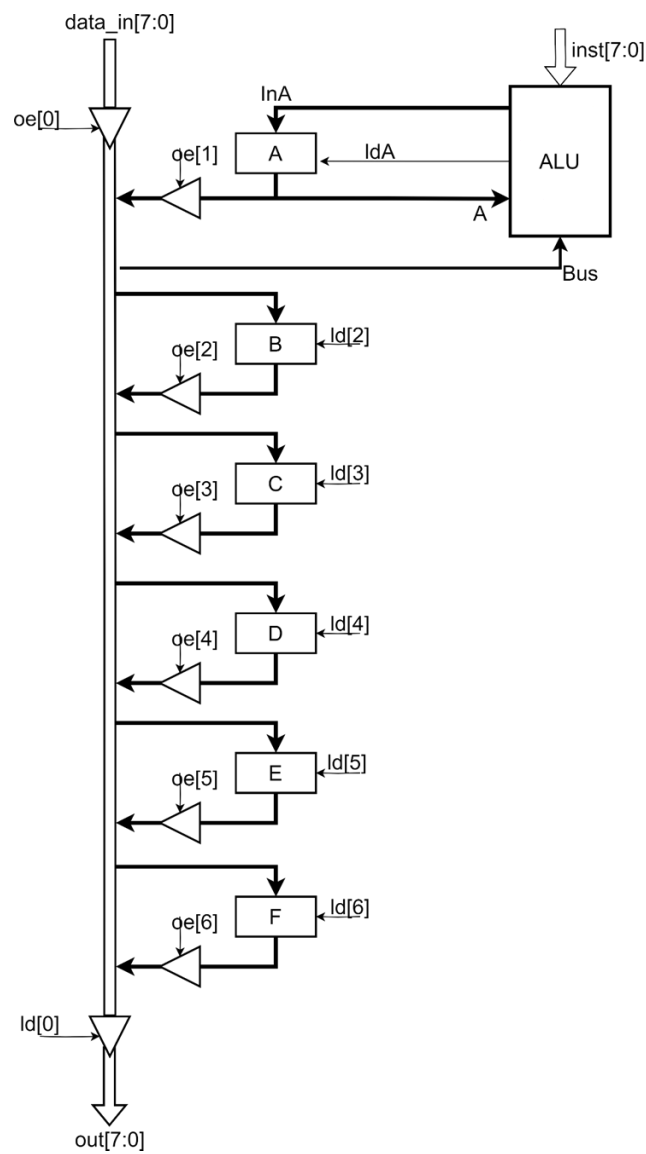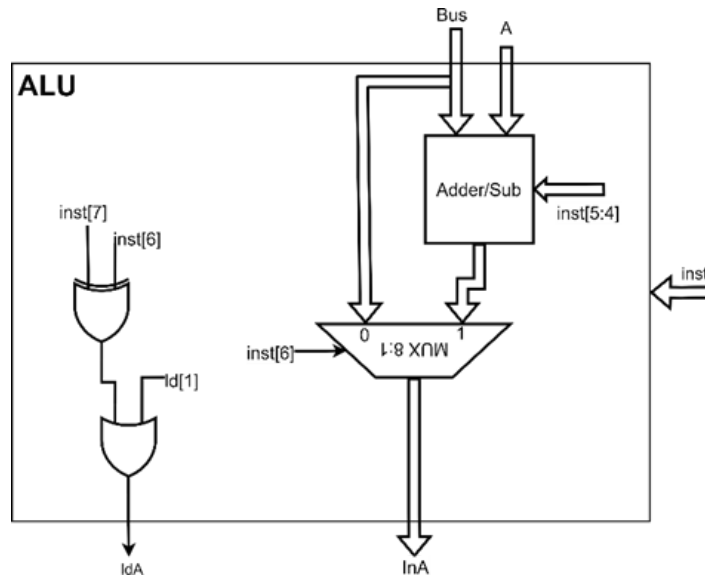


Reg bank architecture

Instruction Set:

Inst[7:6]	Inst[5:3]	Inst[2:0]	Operation
00	DDD	000	IN D $D \leftarrow \text{input}$
00	DDD	SSS	Mov D,S $D \leftarrow S$
00	000	SSS	OUT S $\text{output} \leftarrow S$
01	0XX	S	ADD S $A \leftarrow A+S$
01	1XX	S	SUB S $A \leftarrow A-S$

➤ Schematic diagram

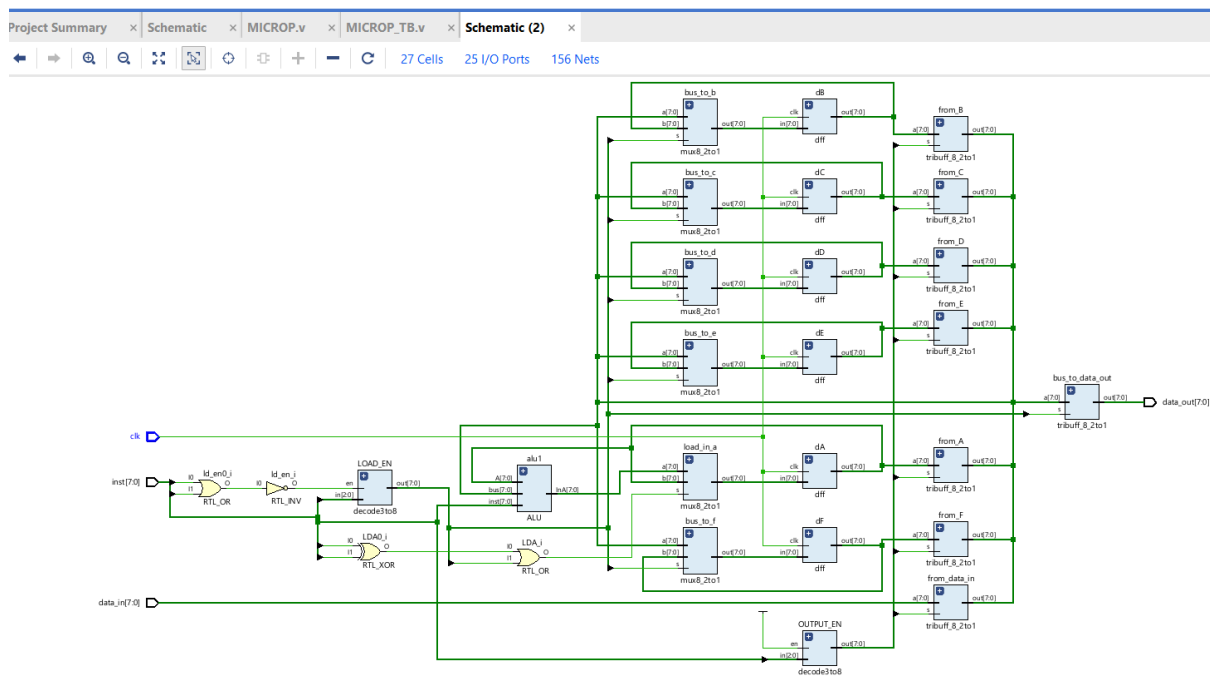

➤ Waveforms:

